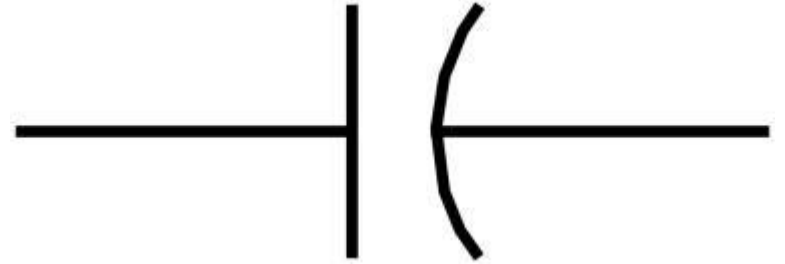


Chapter 5 – Part 2



AC – Bridges

Comparison Bridges

Capacitance

Measurements

1

5.5 AC - BRIDGES

AC - Bridges enable us to perform precise *measurements for the following* :

- Reactance (**capacitance** and **inductance**) measurements.
- Determining the (***Q-factor*** OR ***D-factor***).
- **Frequency** measurements.
- Testing and analyzing of antenna and transmission line performance

AC BRIDGE

The basic circuit of an ac bridge is exactly the same as the Wheatstone bridge circuit except that **impedances** are used instead of resistances, and the supply is an **ac-source**. Also, the null detector must be an **ac instrument**.

Principle

The bridge offset voltage can be found as:

$$\Delta V = \left(\frac{Z_3}{Z_1 + Z_3} - \frac{Z_4}{Z_2 + Z_4} \right) V$$

For balancing condition: ($\Delta V=0$)

Therefore, $Z_1 \cdot Z_4 = Z_2 \cdot Z_3$

For AC-bridges, the null-condition is only valid if V_a and V_b are **equal in amplitude and also same in-phase**.

Substituting $Z_i = Z_i \angle \theta_i$,

$$Z_2 Z_3 \angle (\theta_2 + \theta_3) = Z_1 Z_4 \angle (\theta_1 + \theta_4)$$


* **First** balance condition $\Rightarrow Z_2 Z_3 = Z_1 Z_4$

=amplitude


* **2nd** balance condition $\Rightarrow \angle (\theta_2 + \theta_3) = \angle (\theta_1 + \theta_4)$

in-phase


Structure

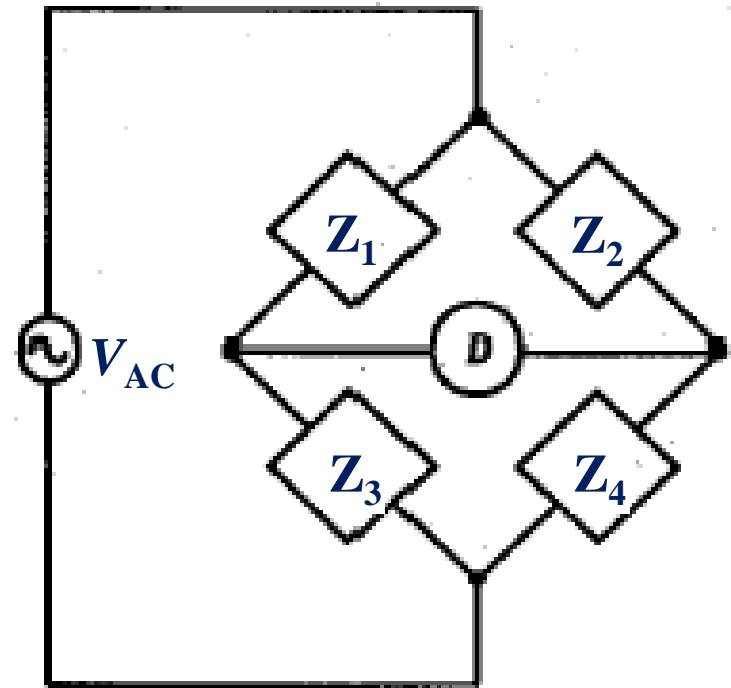


EXAMPLE : V_A AND V_B

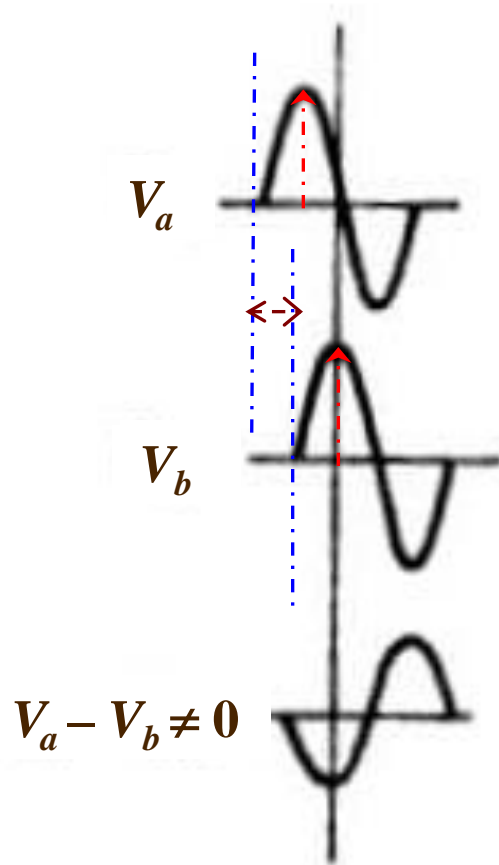

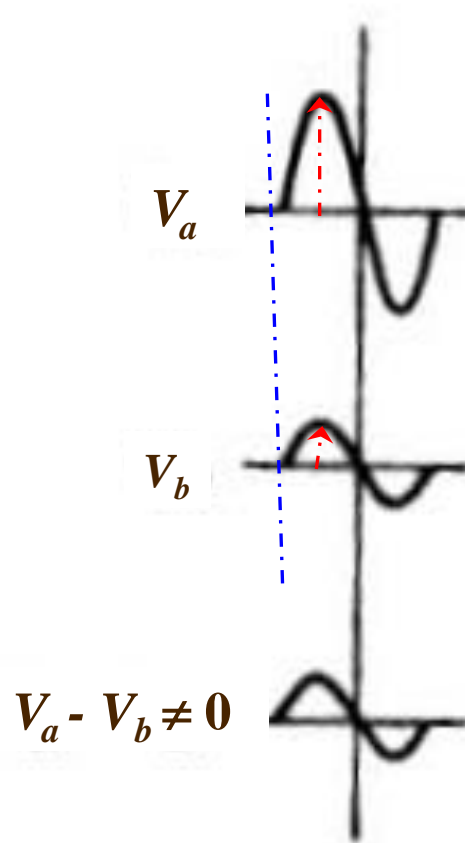V_a and V_b are equal in amplitude but not in-phase.



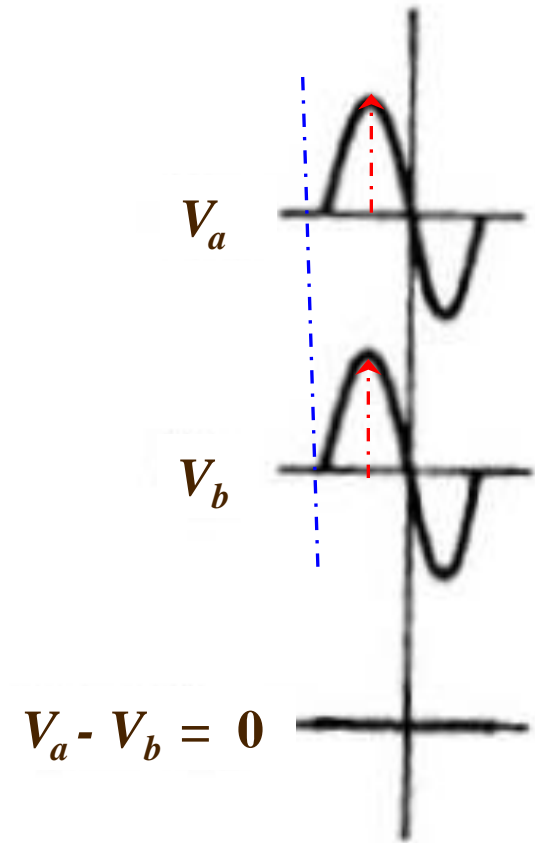V_a and V_b are equal in-phase but not equal in amplitude.



V_a and V_b are equal in amplitude and in-phase.


EXAMPLE 7

The impedances of the bridge arms are

$$Z_1 = 200\Omega\angle 30^\circ \quad ; \quad Z_2 = 150\Omega\angle 0^\circ$$

$$Z_3 = 250\Omega\angle -40^\circ \quad ; \quad Z_x = Z_4 = \text{unknown}$$

Determine the values of the unknown arm.

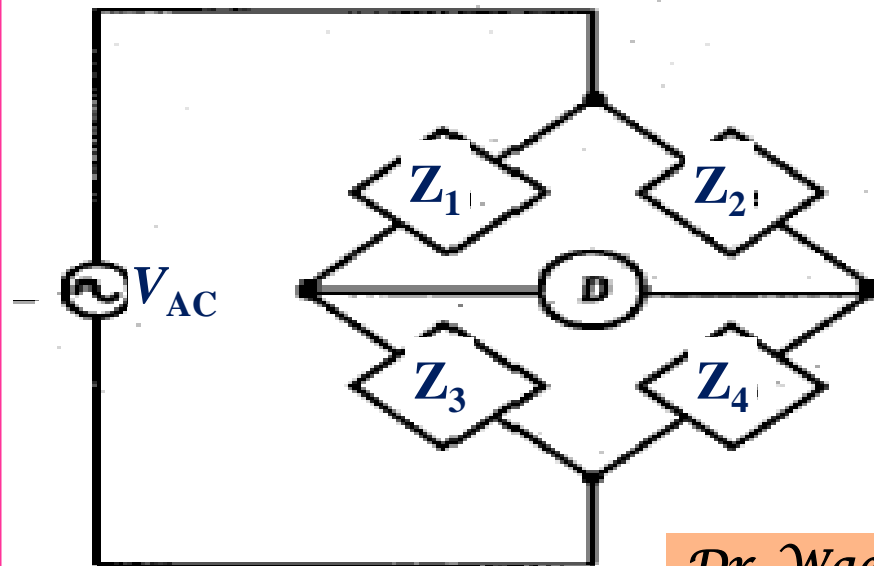

Solution 7

The first condition for balance requires that

$$Z_1 Z_x = Z_2 Z_3 ; \quad \therefore Z_x = \frac{Z_2 Z_3}{Z_1} = \frac{150\Omega \times 250\Omega}{200\Omega} = 187.5\Omega$$

The second condition for balance requires that the sum of the phase angles of opposite arms should be equal

$$\angle\phi_1 + \angle\phi_x = \angle\phi_2 + \angle\phi_3 ; \quad \therefore \phi_x = \phi_2 + \phi_3 - \phi_1 = 0^\circ + (-40^\circ) - 30^\circ = -70^\circ$$

Hence the unknown arm impedance Z_x can be written as

$$Z_x = 187.5\Omega \angle -70^\circ = (64.13 - j176.19)\Omega$$

Where, $Z_x = x + j y = \mathbf{R + j X}$

$$x = r \cos \varphi = 187.5 \cos (-70) = \mathbf{64.13}$$

$$y = r \sin \varphi = 187.5 \sin (-70) = \mathbf{-176.19}$$

CAPACITORS EQUIVALENT CIRCUITS

Capacitor Equivalent Circuits:

The equivalent circuit of a capacitor consists of a pure capacitance C and a resistance R .

Where, C_p represents the actual capacitance value, and R_p represents the resistance of the *dielectric* or *leakage resistance*.


- ❖ Capacitors with a **high-resistance** dielectric are best represented by a **series RC** circuit,
- ❖ Capacitors with a **low-resistance** dielectric represented by the **parallel RC** circuit.

The series impedance is

$$Z_s = R_s - \frac{j}{\omega C_s}$$

The parallel admittance is

$$Y_p = \frac{1}{R_p} + j \omega C_p$$

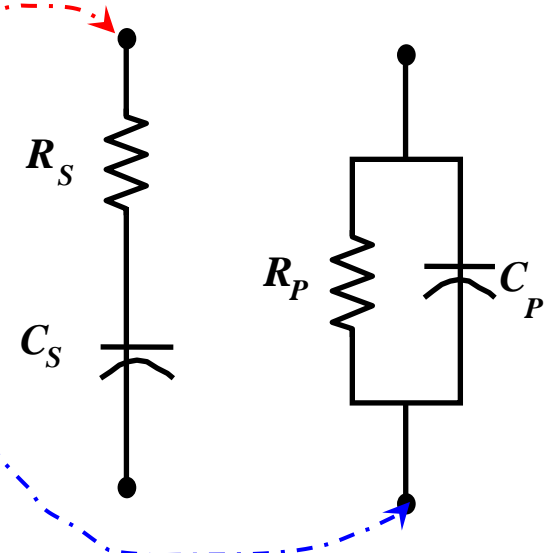

D-FACTOR OF A CAPACITOR

The quality of a capacitor can be expressed in terms of its power dissipation.

A very pure capacitor has a high dielectric resistance (low leakage current) and virtually zero power dissipation.


The *dissipation factor* or *D-factor* is simply the ratio of the component reactance (at a given frequency) to the resistance measurable at its terminals.

For a parallel equivalent circuit

$$D = \frac{X_p}{R_p} = \frac{1}{\omega C_p R_p}$$

For a series equivalent circuit

$$D = \frac{R_s}{X_s} = \omega C_s R_s$$

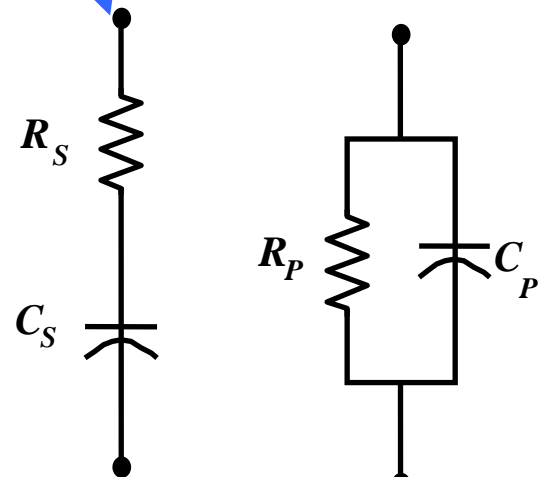

INDUCTORS EQUIVALENT CIRCUITS

Inductor Equivalent Circuits:


- The series equivalent circuit represents an inductor as a pure inductance L_S , in series with the resistance of its coil R_S .
- This **series** equivalent circuit is normally **the best way to represent an inductor**, because the actual winding resistance is involved and this is an important quantity.
- The parallel RL equivalent circuit for an inductor can also be used.

The series impedance is

$$Z_S = R_S + j\omega L_S$$

The parallel admittance is
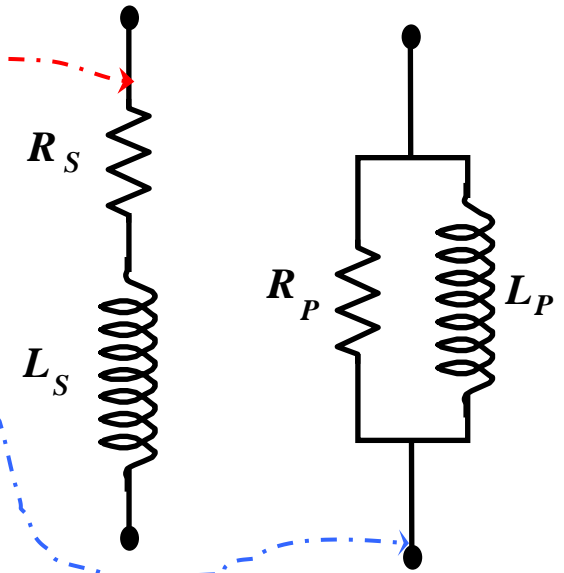
$$Y_P = \frac{1}{R_P} - \frac{j}{\omega L_P}$$



Q - FACTOR OF AN INDUCTOR

The quality of an inductor can be defined **in terms of its power dissipation**.

An ideal inductor should have **zero winding resistance**, and therefore **zero power dissipated** in the winding.


The *quality factor* or *Q-factor*, of the inductor is the *ratio* of its **inductive reactance** to **its resistance** at the op

For a series equivalent circuit:

$$Q = \frac{X_s}{R_s} = \frac{\omega L_s}{R_s}$$

For a parallel equivalent circuit :
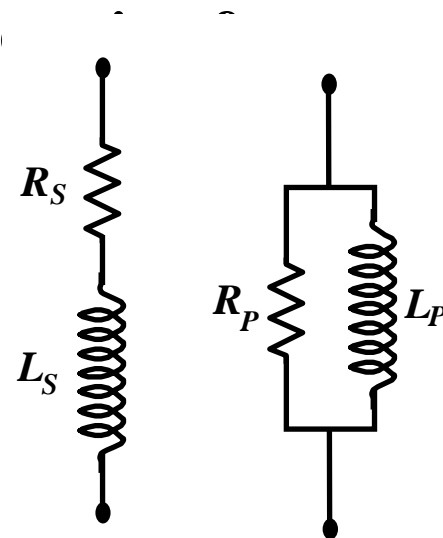
$$Q = \frac{R_p}{X_p} = \frac{R_p}{\omega L_p}$$



5.6.1. CAPACITANCE COMPARISON BRIDGES

- i) **Series-Resistance Capacitance Bridge** (also known as **Similar-angle bridge**)
- The **unknown** capacitance C_s is represented in **series** with resistance R_s .
 - A standard adjustable resistance R_1 is connected in series with C_1 .
 - To obtain a bridge balance, resistors R_1 and either C_1 are adjusted alternately.

The impedances are:


$$Z_1 = R_1 - \frac{j}{\omega C_1} \quad ; \quad Z_3 = R_3$$

$$Z_2 = R_s - \frac{j}{\omega C_s} \quad ; \quad Z_4 = R_4$$

When the bridge is balanced:

$$Z_1 \cdot Z_4 = Z_2 \cdot Z_3$$
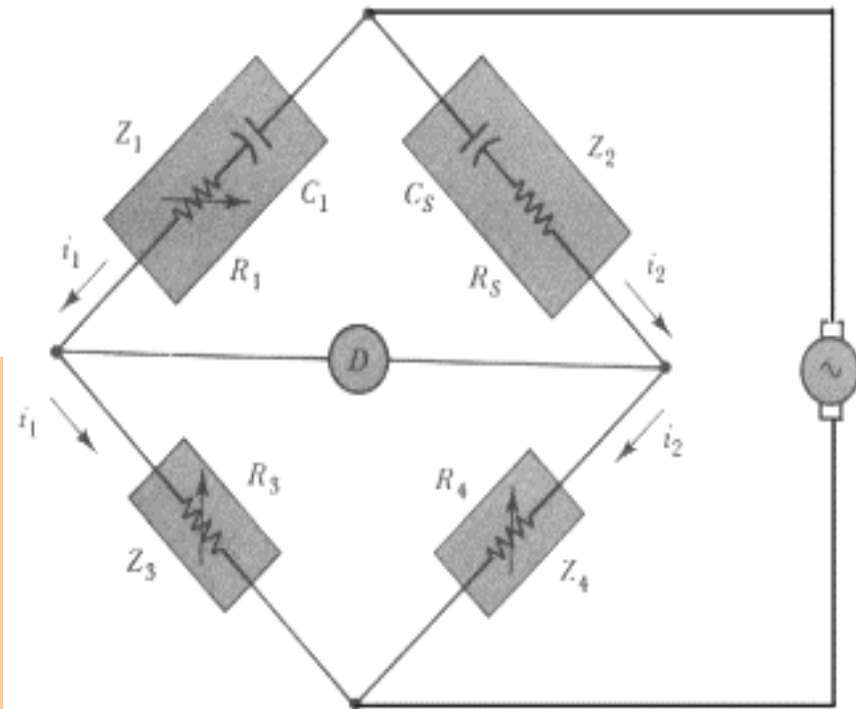
$$\left[R_1 - \frac{j}{\omega C_1} \right] \cdot R_4 = \left[R_s - \frac{j}{\omega C_s} \right] \cdot R_3$$



1. CAPACITANCE BRIDGES

Then the equation is simplified as:

$$R_1 R_4 - j \frac{R_4}{\omega C_1} = R_s R_3 - j \frac{R_3}{\omega C_s}$$

After equating the real terms for both sides, we get:

$$R_1 R_4 = R_s R_3 \quad \longrightarrow \quad R_s = \frac{R_1 R_4}{R_3}$$

And by equating the Imaginary terms both sides, we get :

$$j \frac{R_4}{\omega C_1} = j \frac{R_3}{\omega C_s} \quad \longrightarrow \quad C_s = \frac{C_1 R_3}{R_4}$$

EXAMPLE


A series resistance-capacitance bridge as shown below has a $0.1\mu F$ standard capacitor for C_1 , and $R_3=10k\Omega$. Balance is achieved with 100Hz supply frequency when $R_1=125\Omega$ and $R_4=14.7k\Omega$. Calculate the *resistive* and *capacitive* components of measured capacitor and its *dissipation factor*.

SOLUTION

$$C_s = \frac{C_1 R_3}{R_4} = \frac{0.1\mu \times 10k}{14.7k} = 0.068\mu F$$

$$R_s = \frac{R_1 R_4}{R_3} = \frac{125 \times 14.7k}{10k} = 183.75\Omega$$
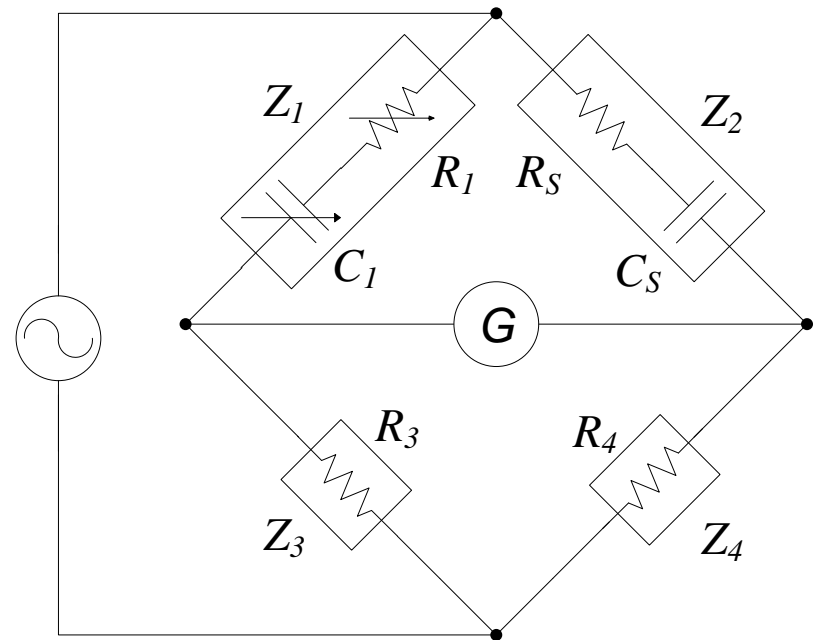
$$D = \omega C_s R_s = 2\pi \times 100 \times 0.068 \times 10^{-6} \times 183.75 = 0.00785$$



II) PARALLEL-RESISTANCE CAPACITANCE BRIDGE (ALSO KNOWN AS SIMILAR-ANGLE BRIDGE)

In this bridge the **unknown capacitance** is represented by its **parallel equivalent circuit**; C_p in parallel with R_p , and Z_3 and Z_4 are resistors.

- The bridge balance is achieved by adjustment of R_1 and C_1 .

The load impedances are:

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1} + j\omega C_1 \quad ; \quad Y_p = \frac{1}{Z_2} = \frac{1}{R_p} + j\omega C_p$$

$$Z_3 = R_3 \quad ; \quad Z_4 = R_4$$

When the bridge is balanced:

$$Z_1 Z_4 = Z_2 Z_3$$


$$\left(\frac{R_1}{1 + j\omega C_1 R_1} \right) \cdot R_4 = \left(\frac{R_p}{1 + j\omega C_p R_p} \right) \cdot R_3$$

After equating the real & Imaginary terms:

$$R_p = \frac{R_1 R_4}{R_3}$$

and

$$C_p = \frac{C_1 R_3}{R_4}$$

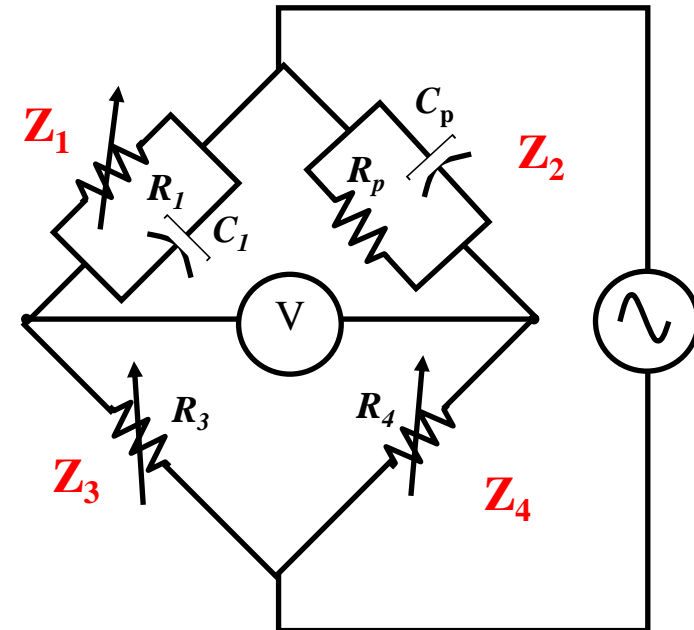

EXERCISE 6

Find the parallel equivalent circuit for C_S and R_S values determined in Example 8. Also determine the component values of R_1 and R_4 required to balance the calculated C_P and R_P values in a parallel resistance-capacitance bridge. Assume that R_3 remains at $10\text{k}\Omega$ and C_1 at $0.1\mu\text{F}$.

SOLUTION EXERCISE 6

EXAMPLE

A parallel-resistance capacitance bridge has a standard capacitance value of $0.1\mu\text{F}$. Balance is achieved at a supply frequency of 100Hz when $R_3 = 10\text{k}\Omega$, $R_1 = 375\text{k}\Omega$, and $R_4 = 14.7\text{k}\Omega$.

Determine the resistive and capacitive components of the measured capacitor and its dissipation factor (*D-factor*).

Solution

For the given parallel-resistance capacitance bridge, find R_p , C_p and the D -factor :-

$$C_P = \frac{C_1 R_3}{R_4} = \frac{0.1 \mu F \times 10 k\Omega}{14.7 k\Omega} = 0.068 \mu F$$

$$R_P = \frac{R_1 R_4}{R_3} = \frac{375 k\Omega \times 14.7 k\Omega}{10 k\Omega} = 551.3 k\Omega$$

The dissipation factor is the D -factor

$$D = \frac{1}{\omega C_P R_P} = \frac{1}{2\pi \times 100 \times 0.068 \times 10^{-6} \times 551.3 \times 10^3} \approx 42.5 \times 10^{-3}$$